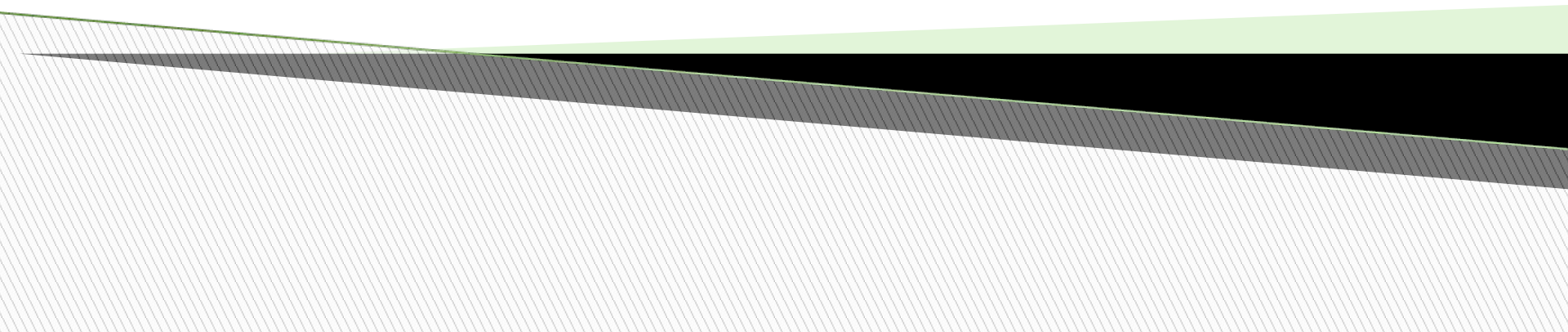



Oscillator



INTRODUCTION:

- An oscillator is an electronic circuit that gives an output without any input signal.
- It comprises active and passive circuit elements and sinusoidal produces repetitive waveforms at the output *without the application of a direct external input signal to the circuit.*
- *It* converts the dc power from the source to ac power in the load. A rectifier circuit converts ac to dc power, but an oscillator converts dc noise signal/power to its ac equivalent.
- The general form of a harmonic oscillator is an electronic amplifier with the output attached to a narrow-band electronic filter and the output of the filter attached to the input of the amplifier.

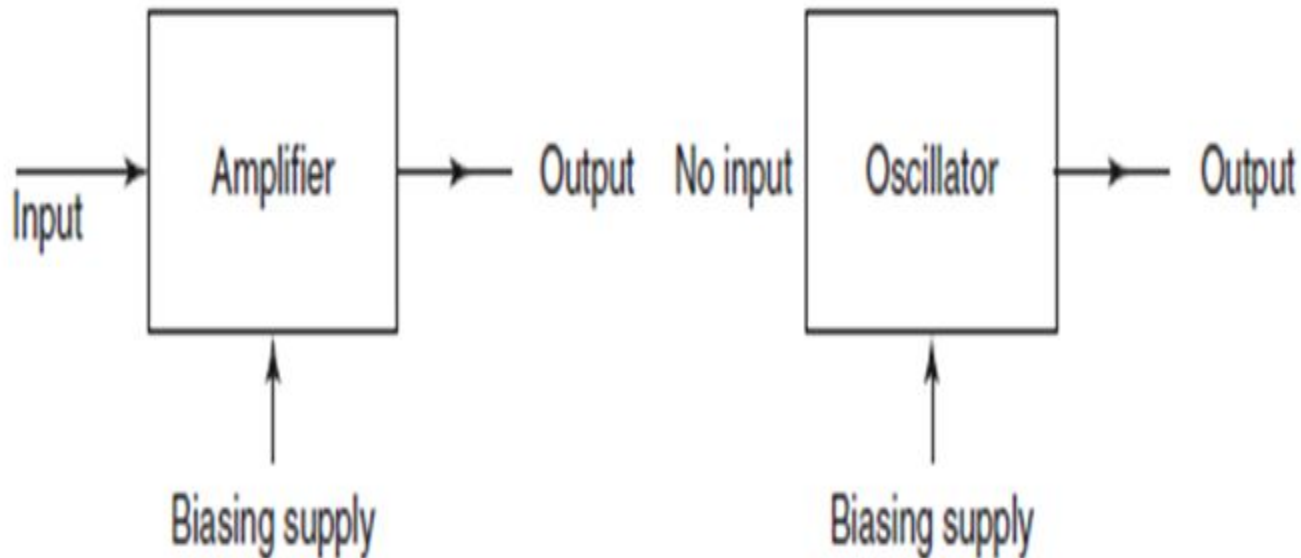Difference between an amplifier and an oscillator:



Schematic block diagrams showing the difference between an amplifier and an oscillator

CLASSIFICATIONS OF OSCILLATORS:

- Oscillators are classified based on the type of the output waveform.
- If the generated waveform is *sinusoidal* or close to sinusoidal (with a certain frequency) then the oscillator is said to be a Sinusoidal Oscillator.
If the output waveform is *non-sinusoidal*, which refers to square/saw-tooth waveforms, the oscillator is said to be a Relaxation Oscillator.
- An oscillator has a positive feedback with the loop gain infinite.
-

CONDITIONS FOR OSCILLATION: BARKHAUSEN CRITERIA

Earlier we established that the overall gain of a feedback amplifier is $A_f = A/(1 + A\beta)$, where A is the gain of the internal amplifier, β is the feedback ratio, and $-A\beta$ is the loop gain. For positive feedback, the feedback gain is expressed as:

$$A_f = \frac{A}{1 - A\beta}$$

For $A\beta = 1$, Eq. yields $A_f = \infty$. The amplifier then produces an output voltage without any externally applied input voltage. Thus, the amplifier becomes an oscillator. When the signal equals $V_o' \Rightarrow A\beta V_o = V_o$ or $A\beta = 1$, the output voltage regenerates itself and the amplifier oscillates. This condition is called the Barkhausen criterion. This condition means that $|A\beta| = 1$ and the phase angle of $A\beta$ is zero or an integral multiple of 360. The basic conditions for oscillation in a feedback amplifier are: (1) the feedback must be regenerative, (2) the loop-gain must be unity, and (3) the phase difference must be zero or an integral multiple of 360.

CLASSIFICATIONS OF OSCILLATORS:

- The classification of various oscillators is shown in the table

Different types of oscillators and their frequency ranges

<i>Type of Oscillator</i>	<i>Frequency Range Used</i>
1. Audio-frequency oscillator	20 Hz – 20 kHz
2. Radio-frequency oscillator	20 kHz – 30 MHz
3. Very-high-frequency oscillator	30 MHz – 300 MHz
4. Ultra-high-frequency oscillator	300 MHz – 3 GHz
5. Microwave oscillator	3 GHz – 30 GHz
6. Millimeter wave oscillator	30 GHz – 300 GHz


CHARACTERISTICS OF OSCILLATORS:

- Oscillators are a common element of almost all electronic circuits. They are used in various applications, and their use makes it possible for circuits and subsystems to perform numerous useful functions.
- In oscillator circuits, oscillation usually builds up from zero when power is first applied under linear circuit operation.
- The oscillator's amplitude is kept from building up by limiting the amplifier saturation and various non-linear effects.
- Oscillator design and simulation is a complicated process. It is also extremely important and crucial to design a good and stable oscillator.
- Oscillators are commonly used in communication circuits. All the communication circuits for different modulation techniques—AM, FM, PM—the use of an oscillator is must.
- Oscillators are used as stable frequency sources in a variety of electronic applications. (Quartz watches)
- Oscillator circuits are used in computer peripherals, counters, timers, calculators, phase-locked loops, digital multi-metres, oscilloscopes, and numerous other applications.


CRYSTAL OSCILLATOR:

- ❑ Crystal oscillator is most commonly used oscillator with high-frequency stability. They are used for laboratory experiments, communication circuits and biomedical instruments. They are usually fixed frequency oscillators where stability and accuracy are the primary considerations.
- ❑ In order to design a stable and accurate LC oscillator for the upper HF and higher frequencies it is absolutely necessary to have a crystal control; hence, the reason for crystal oscillators.
- ❑ Crystal oscillators are oscillators where the primary frequency determining element is a quartz crystal. Because of the inherent characteristics of the quartz crystal the crystal oscillator may be held to extreme accuracy of frequency stability. Temperature compensation may be applied to crystal oscillators to improve thermal stability of the crystal oscillator.
- ❑ The crystal size and cut determine the values of L , C , R and C' . *The resistance R is the friction of the vibrating crystal, capacitance C is the compliance, and inductance L is the equivalent mass. The capacitance C' is the electrostatic capacitance between the mounted pair of electrodes with the crystal as the dielectric.*

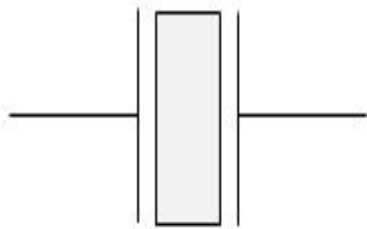Equivalent Circuit Diagram of Piezoelectric Crystal :



(a)

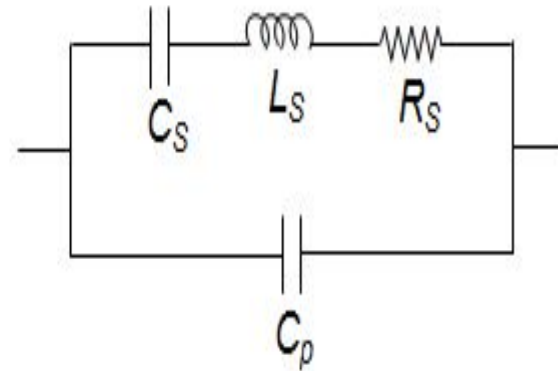

(b)

Figure (a) Quartz Crystal (b) Equivalent Electric Circuit

Due to the presence of C_p , the crystal will resonate at two different frequencies viz.,



1. Series Resonant Frequency, f_s which occurs when the series capacitance C_s resonates with the series inductance L_s . At this stage, the crystal impedance will be the least and hence the amount of feedback will be the largest. Mathematical expression for the same is given as

$$f_s = \frac{1}{2\pi\sqrt{L_s C_s}}$$

2. Parallel Resonant frequency, f_p which is exhibited when the **reactance** of the $L_s C_s$ leg equals the reactance of the **parallel capacitor** C_p i.e. L_s and C_s resonate with C_p . At this instant, the crystal impedance will be the highest and thus the feedback will be the least. Mathematically it can be given as

$$f_p = \frac{1}{2\pi\sqrt{L_s \frac{C_p C_s}{C_p + C_s}}}$$

Circuit Diagram of crystal oscillator:

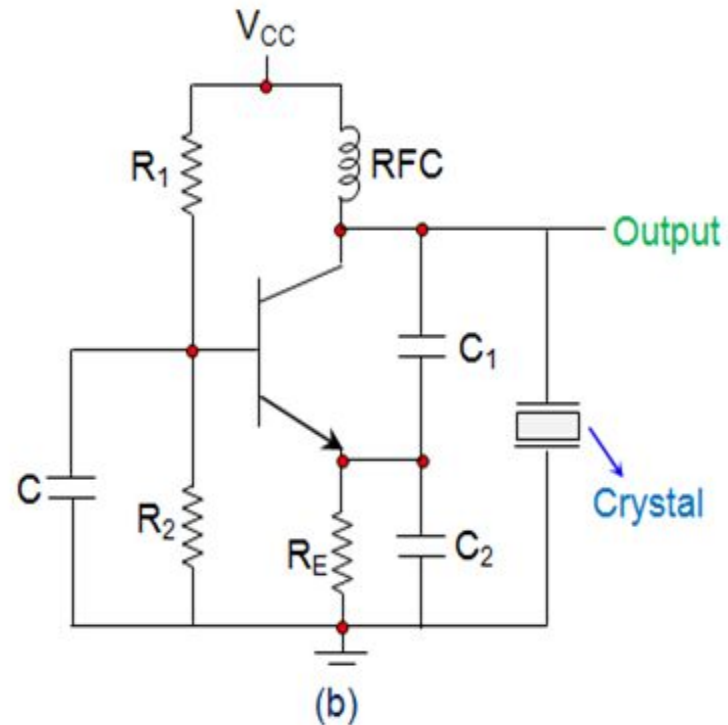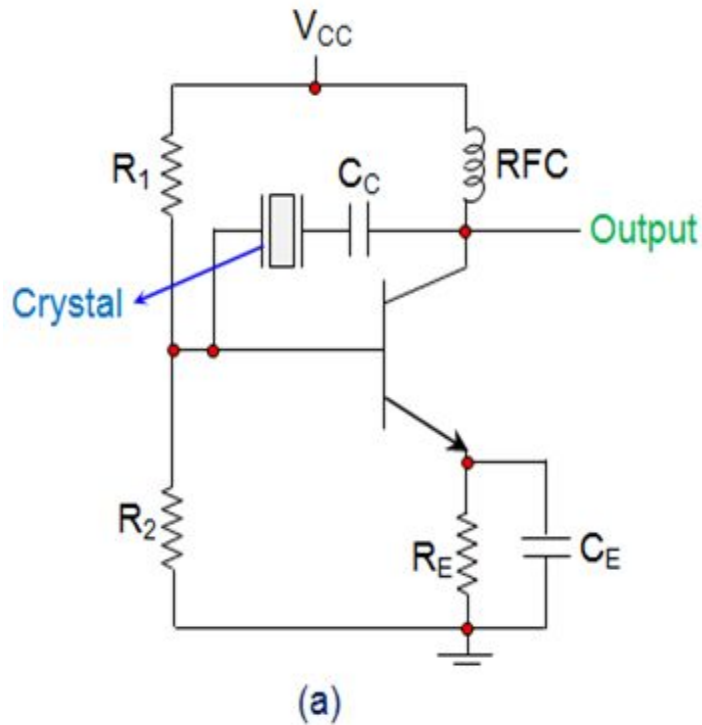

Crystal Oscillator Operating in (a) Series Resonance (b) Parallel Resonance

Operation of Crystal Oscillator:

- In the circuits shown, the resistors R_1 and R_2 form the voltage divider network while the emitter resistor R_E stabilizes the circuit. Further, C_E acts as an AC bypass capacitor while the coupling capacitor C_C is used to block DC signal propagation between the collector and the base terminals.
- Next, the capacitors C_1 and C_2 form the capacitive voltage divider network . In addition, there is also a Radio Frequency Coil (RFC) in the circuits which offers dual advantage as it provides even the DC bias as well as frees the circuit-output from being affected by the AC signal .
- On supplying the power to the oscillator, the amplitude of the oscillations in the circuit increases until a point is reached wherein the nonlinearities in the amplifier reduce the loop gain to unity. Next, on reaching the steady-state, the crystal in the feedback loop highly influences the frequency of the operating circuit. Further, here, the frequency will self-adjust so as to facilitate the crystal to present a reactance to the circuit such that the Barkhausen phase requirement is fulfilled.
- The typical operating range of the crystal oscillators is from 40 KHz to 100 MHz

Advantages of Crystal Oscillator:

- The crystal oscillator has very low frequency drift due to change in temperature and other parameters.
- The crystal oscillator Q is very high.
- It has Automatic amplitude control.
- It has very high frequency **stability**.
- The crystal oscillator is possible to obtain very high precise and **stable** frequency of oscillators.



Disadvantages of crystal oscillator:

- Crystals of low fundamental frequencies are not easily available.
- These are suitable for high frequency application.

Applications of crystal oscillator:

- The crystal oscillators are used in radio and TV transmitters.
 - It is used as a crystal clock in microprocessors.
 - It is used in the frequency synthesizers.
 - It is used in special types of receivers.
- 